Answers and marking guidance

Award one mark per correct, developed point unless stated. Other valid answers should be credited.

2 Complete the truth table for Z.

- A B Z: 0 0 1; 0 1 0; 1 0 0; 1 1 0
- (This is a NOR gate)

3 Quick check

- a) 0
- b) 1
- c) 8

4 Key terms

- 1 – A
- 2 – C
- 3 – B

5 Explain what is meant by ‘Rows in a 3-input truth table’.

- 8