

N5 Analogue Electronics – Voltage Divider Worksheet

In your jotter, draw the following circuits and calculate the missing value.
You can verify your answers with Yenka.


Q1

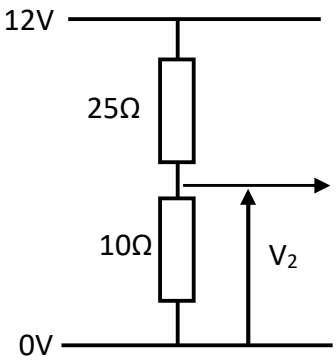


Q2

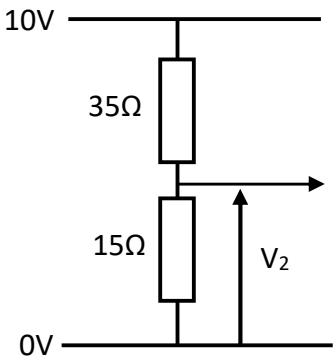


Q3

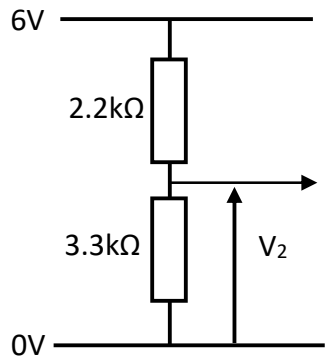


Q4

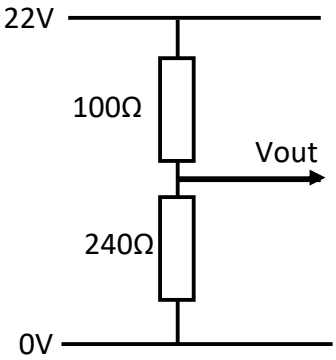


Q5

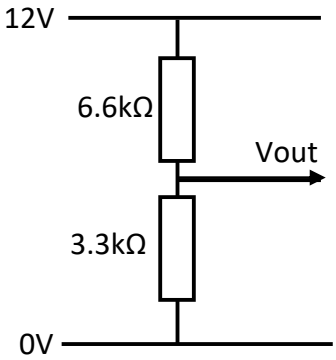


Q6

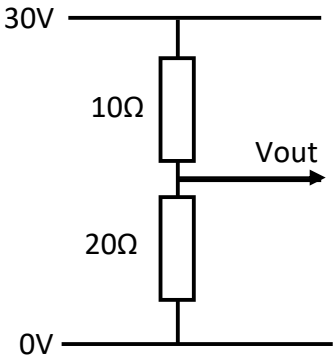


Q7

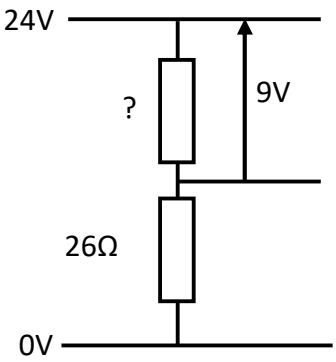


Q8

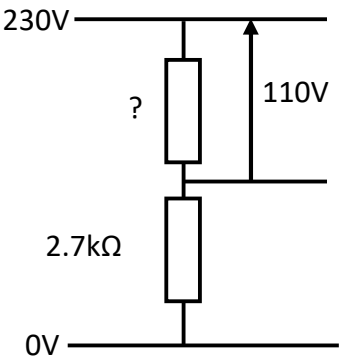


Q9

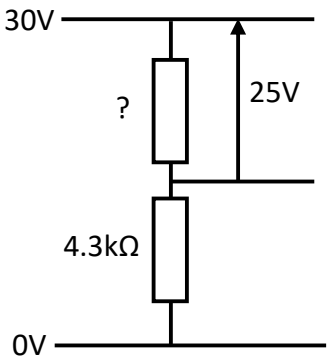

Q10

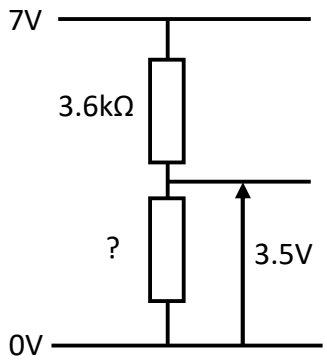

Q11

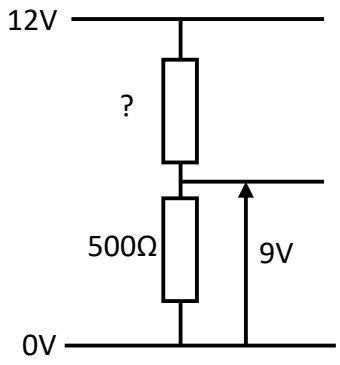

Q12

