Digital logic

National 5 · Electronics & control · Answers

Answers and marking guidance

Award one mark per correct, developed point unless stated. Other valid answers should be credited.

2 Complete the truth table for Z.

- A B Z: 0 0 1; 0 1 0; 1 0 0; 1 1 0

3 Quick check

- a) $Z = (\bar{A} + B) \cdot C$
- b) 1
- c) 0
- d) 0

4 Key terms

- 1 – C
- 2 – A
- 3 – B

5 Explain what is meant by ‘NOT gate’.

- Output is the opposite of the input.

6 Explain what is meant by ‘Rows in a 3-input truth table’.

- 8