Components, Ohm's law & resistor networks

ENGINEERING WITH MR KELLY

Higher · Electronics & control · Worksheet

Name _____ Class _____ Date _____

By the end of this worksheet I can…

- ☐ recognise and draw standard component symbols
- ☐ use Ohm's law and the power formulae
- ☐ calculate total resistance of series and parallel resistors
- ☐ show where an ammeter (series) and voltmeter (parallel) are connected
- ☐ describe advantages of simulating a circuit before building it

I DO — Worked example

Read how a full-mark answer is built

A pupil wants to simulate a circuit before building it.

1 Explain one advantage of simulating the circuit before constructing it. (2 marks)

Full-mark answer each ✓ is one mark

Faults in the circuit can be found and corrected on screen before it is built ✓, so no components are damaged or wasted ✓.

Why marks are not awarded

"It is cheaper and it is quicker."

0 marks: two vague benefits, no cause and effect.

WE DO — Guided practice

Use the starters and word bank to help you

Two 470 Ω resistors are connected in parallel.

2 Calculate the total resistance. (2 marks)

Sentence starters

One … is …, which means …

Another … is …, so …

Word bank

Tip: 2 marks = 2 separate, developed points.

YOU DO **On your own** No notes. Check your answers afterwards.

3 Quick check: tick one box for each.

a) An ammeter is connected...
☐ In parallel ☐ In series ☐ Across the supply ☐ Anywhere

b) 5 V across 470 Ω: the power is about...
☐ 0.053 W ☐ 2350 W ☐ 94 W ☐ 0.011 W

c) As light increases, an LDR's resistance...
☐ Rises ☐ Falls ☐ Stays the same ☐ Becomes zero

d) Two 1 kΩ resistors in parallel have a total resistance of...
☐ 2 kΩ ☐ 1 kΩ ☐ 500 Ω ☐ 250 Ω

4 Key terms: write the letter of the matching description next to each term.

1. **Ohm's law**	____	**A**	Resistance falls as light level rises.
2. **Electrical power**	____	**B**	Resistance falls as temperature rises.
3. **Series resistors**	____	**C**	$V = I \times R$
4. **Parallel resistors**	____	**D**	$P = V \times I$ (also I^2R and V^2/R)
5. **LDR**	____	**E**	R total = R1 + R2 + ...
6. **NTC thermistor**	____	**F**	1/RT = 1/R1 + 1/R2; total is less than the smallest.

A 12 V lamp draws 0.5 A.

5 Calculate the power of the lamp. (2 marks)

An ammeter is needed to measure the current through a lamp.

6 Draw the symbol for an ammeter and state how it is connected. (2 marks)

In a series circuit with R1 and R2, R1 is increased.

7 State the effect on V1 and on the current. (2 marks)

Check and reflect

Mark your answers with the answer sheet. Go back to the checklist on the site and re-rate each “I can” statement above. Which one still needs work?